

TABLE OF CONTENTS

PART 1

<u>Circuits, Contactors, Capacitors, Solenoids, Relays, Rheostats, Transistors, Potentiometers, Diodes, LED's, Grounds, Ground Loops, Resistors, Limit Switches and Proximity Sensor</u>	<u>.Page</u>
What Do They Look Like, How Do They Work And Where Are They Used...	1-1
Types Of Structure-Ground.....	1-2
Types Of Contactors	1-2
Battery Contactors	1-2
Schematics And Pictorials Of Typical Battery Contactor Circuits.....	1-3, 4
Schematics And Pictorials Of Typical Starter Contactor Circuits.....	1-5, 6
Solenoids.....	1-7
Relays.....	1-8
Schematics And Pictorials Of Typical Relay Circuits.....	1-9
Rheostats	1-10
Schematics And Pictorials Of Typical Rheostat Circuits	1-11
Potentiometers.....	1-12
Schematics And Pictorials Of Typical Potentiometer (fader) Control Circuits.....	1-13
Diodes	1-14
Schematics And Pictorials Of Typical Diode Uses	1-15, 16, 17, 19
Diodes: Light Emitting Diodes.....	1-20
Transistors NPN, PNP	1-21
Schematics And Pictorials Of Typical PNP Transistorized Light Dimming Circuits.....	1-22
Transistors: NPN.....	1-23
Schematics And Pictorials Of Typical NPN Transistorized Light Dimming Circuits	1-24
The Limit Switch (microswitch)	1-25
Limit Switch Uses	1-26
Schematic/Pictorial Of Advanced Uses Of Limit Switches.....	1-27
Proximity Sensor Switch.....	1-28
How Does The Proximity Sensor Switch Work.....	1-28
Operation Of The Door Lock Proximity Sensing Circuit.....	1-29
Test Questions And Answers About the Door Lock Proximity Sensing Circuit.....	1-30

PART 2

Basic Types Of Circuits

Page

What Are They And What Makes Them Different...	2-1
Basic Types Of Circuits.....	2-2
Why Are Circuits Classified.....	2-2
Power Circuits.....	2-2
Load Circuits, Control Circuits, Indicating Circuits, Combination Circuits.....	2-3,4
Examples Of:	
Basic "Power" Circuits.....	2-5
Power Circuit, Current Limiter.....	2-6, 7
Basic "Load" Circuits.....	2-8, 9
Basic "Controlling" Circuits.....	2-10, 11
Basic "Indicating" Circuits.....	2-12, 13, 14
Basic "Combination" Circuits.....	2-15, 16, 17
Examples Of Common Circuits On Most Aircraft With Their Corresponding Main Circuit Types	2-18

PART 3

The Voltmeter

Page

Developing The Fundamentals...	3-1
The Voltmeter: Introduction And Principles	3-2
Exception To The Concept: No Current Flow And/Or No Resistance—	
No Voltage Drop Across A Load.....	3-3
Voltmeter: Measuring Across Broken (open) Components.....	3-4, 5
Voltmeter Principles Across An Open.....	3-6
Voltmeter Definitions: Voltage, Voltage Drop, Potential Difference, Load	3-7
Voltmeter Hookup	3-8
Polarity Of A Load And Current Flow	3-9
Polarity Of A Load, Current Flow And Voltage Drop Using A DMM.....	3-10, 11, 12, 13, 14, 15
Summary: Voltmeters, Schematics And Pictorials	3-16

PART 4A

<u>Constant Voltage Section Concept</u>	Page
Developing Ones Electrical Sense...	4A-1
Developing Ones <i>Electrical Sense</i> Through The "Constant Voltage Section" Concept	4A-2
<i>Electrical Sense</i> —How Can It Be Achieved?	4A-2
Definitions: Constant Voltage Section, Segment, Item, Identical Electrical Point (I.E.P.), Reference Point, Input Side, Output Side.....	4A-3, 4
Circuit Examples Of The "Constant Voltage Section" (C.V.S.) Concept	4A-5
"Constant Voltage Sections" Identified: Circuit 4A-A1	4A-6
"Items" Within Constant Voltage Sections: Circuit 4A-A2	4A-7
"Segments" and "Items" Within Constant Voltage Sections: Circuit 4A-A3.....	4A-8
"Segments" Within Constant Voltage Sections Identified: Circuit 4A-A3	4A-9
"Segments" Within Constant Voltage Sections: Circuit 4A-A4.....	4A-10
"Segments" Within Constant Voltage Sections: Circuit 4A-A5.....	4A-11
"Identical Electrical Points" (I.E.P.)— <u>The Concept</u>	4A-12
"Identical Electrical Points" Within Constant Voltage Sections Identified: Circuit 4A-A6	4A-13
Identify "Constant Voltage Sections" With A Voltmeter: Circuit 4A-B1	4A-14
Using A Voltmeter, Measure "C.V.S.s" At Their Respective I.E.P.s: Circuit 4A-B1.....	4A-15
Identify 'Segments' Within Constant Voltage Sections: Circuit 4B-B2.....	4A-16
Using A Voltmeter, Measure "C.V.S.s" At Their Respective I.E.P.s: Circuit 4A-B1 Answers.....	4A-17
Identify "Segments", Their "C.V.S.s", And Any Singular C.V.S.s: Circuit 4A-B3	4A-18
Identify All C.V.S.s, Their Respective "Segments" And Any Sole C.V.S.s: Circuit 4A-B4.....	4A-19
Identify "Identical Electrical Points" Within A Constant Voltage Section: Circuit 4A-B5	4A-20
Identify C.V.S.s Attached to "I.E.P.s": Circuit 4A-B5.....	4A-21
Identify "Identical Electrical Points" Within A C.V.S.s: Circuit 4A-B6 Answers.....	4A-22
Identifying C.V.S.'s With A Voltmeter: Circuit 4A-B7	4A-23
Identifying C.V.S.'s With A Voltmeter: Circuit 4A-B7.....	4A-24
Identifying C.V.S.'s With A Voltmeter: Circuit 4A-B7 Answers.....	4A-25

PART 4B

Constant Voltage Section Concept

Page

Identifying Constant Voltage Sections, Their Segments And Their Identical Electrical Points...

How To Label Constant Voltage Sections, Segments, And Their I.E.P.'s	4B-1
Identifying Constant Voltage Sections Circuit 4B-A1	4B-2
Specific Labeling Of Constant Voltage Sections, Segments And Their I.E.P.'s	4B-3
How To Label Identical Electrical Points (I.E.P.'s)	4B-4
Examples Of Constant Voltage Sections, Segments And Their I.E.P.'s Ckt. 4B-B	4B-5
The Following Comprise C.V.S.'s, Segments And Their I.E.P.'s	4B-6
Explanations For C.V.S.'s, Segments And Their I.E.P.'s	4B-7
Examples Of Constant Voltage Sections, Segments And Their I.E.P.'s 4B-C	4B-8
The Following Comprise C.V.S.'s, Segments And Their I.E.P.'s	4B-9
Explanations For C.V.S.'s, Segments And Their I.E.P.'s	4B-10
Examples Of Constant Voltage Sections, Segments And Their I.E.P.'s Ckt. 4B-D	4B-11
The Following Comprise C.V.S.'s, Segments And Their I.E.P.'s	4B-12
Explanations For C.V.S.'s, Segments And Their I.E.P.'s	4B-13
Using The Previous C.V.S.s, Segments And I.E.P.s Of CKT. 4B-A1, Try Following The Four CKT's., As The Wiper Is Moved From OFF To HIGH . Make Note Of Why The C.V.S.s Change.	4B-14
Measure the Voltage Of Each Meter In Circuit 4B-A6	4B-15, 16
In The Appropriate Meter Window, Place Voltage From Circuit 4B-A7	4B-17
Voltage Answers Plus Explanations for Circuit 4B-A8	4B-18
	4B-19

PART 5

Constant Voltage Section Concept, The Voltmeter And Ohm's Law

Page

Introduction To Using A Combination Of The Constant Voltage Section Concept, A Voltmeter And Ohm's Law To Determine A Voltage...

Using A Combination Of C.V.S.s, Voltmeters And Ohm's Law To Determine A Voltage	5-1
What To Look For While Studying The Following Five Examples	5-2
Battery, Lamp, Resistor Circuits: 5-A1	5-3
Answers And Explanations For 5-A1	5-4
Battery, Lamp, Resistor Circuits: 5-A2	5-5

Answers And Explanations For 5-A2	5-6
Battery, Lamp, Resistor Circuits 5-B.....	5-7
Answers And Explanations For 5-B	5-8
Battery, Lamp, Resistor Circuits 5-C.....	5-9
Answers And Explanations For 5-C	5-10, 11
Battery, Lamp, Resistor Circuits 5-D	5-12
Answers And Explanations For 5-D	5-13

PART 6A

Troubleshooting With A Voltmeter

Page

Developing The Fundamentals...

6A-1

Troubleshooting With A Voltmeter: Fundamentals 6A-2

Single-Wire and Multi-Ground Wire Electrical Systems 6A-2

Single Ground Wire, Series Circuit 6A-A1 6A-3

Multi-Ground Wire, Series Circuit 6A-A2 6A-3

Multi-Ground Wire Parallel Circuit 6A-B1 6A-4

Single-Ground Wire Parallel Circuit 6A-B2..... 6A-4

"What To Know"...The Voltmeter: Prior to Hookup, Its Functions and Concepts 6A-5

Note: Concepts Are Not In Any Particular Order.

Concepts • Voltmeter Placed Across An Open Reads System Voltage 6A-5

• Circuit With Switch In OFF Position 6A-C1 6A-6

• Circuit With Broken (open) Switch 6A-C2 6A-7

• Circuit With Burnt Out Lamp 6A-C3..... 6A-7

• Circuit With Severely Corroded Lamp 6A-C4.....6A-8

• Circuit With Cracked (open) Resistor 6A-D1 6A-8

• Circuit Showing "Open" Voltage Across Battery 6A-D2 6A-9

• Circuit With Broken (open) Wire 6A-E 6A-9

• Voltmeter Leads Placed Across, Closed Hot Switch Reads 0v: Circuit 6A-F1 6A-10

• Voltmeter Placed In Series With A Normal battery Will Read Battery Voltage 6A-11

• Voltmeter Probes Placed On The Battery Post And Its Terminal Reads 0 Volts..... 6A-11

• Voltmeter Leads Placed Across I.E.P.s will read 0 Volts: Circuit 6A-F3..... 6A-11

Concepts	• Voltmeter Placed Between Two Severely Corroded Points Reads A Voltage Drop...6A-12
	• Circuit Showing Volt./Resistance Between Bat. Post/Term. 6A-G1, G2 6A-12
	• Circuits with normal Voltage Drop and Ohmic Value 6A-G3, 6A-G4..... 6A-12
	• Voltmeter To Have Meaning, One Must Know What Is A Normal And Abnormal Value.....6A-13
	• Circuit With Internally Corroded Switch Circuit 6A-H1 6A-13
	• Circuit With Broken (open) Switch Circuit 6A-H2 6A-14
	• Circuit With A Severely Corroded Lamp Input Terminal Circuit 6A-H3 6A-14
	• Locating a Circuit Break Using A Voltmeter..... 6A-15
	• Circuit With Normal Voltage Drops Across Loads Circuit 6A-I1 6A-15
	• Circuit With Normal Voltage Drops But Rearranged Loads Circuit 6A-I2..... 6A-15
	• Voltmeter, Up To The Point Of The Break, Will Read System Voltage; Pass The Break, the Voltage Drops To Zero. <i>Reference</i> Point Is Ground. Circuit 6A-J.....6A-16
	• <i>Reference Point</i> Is Where The Negative Probe Is Place With Respect To The Positive Probe Of The Meter Circuit 6A-K..... 6A-17
	• Illustrated Summary Of The Seven Voltmeter Concepts 6A-18
	• Circuit With The <i>Reference</i> Points At Different Locations Circuit 6A-L1..... 6A-18
	• Illustrated Summary Of The Seven Voltmeter Concepts Continued Ckt.....6A-L2, 6A-19
	• Illustrated Summary Of The Seven Voltmeter Concepts Continued Ckt.....6A-M, 6A-20

PART 6B

<u>Troubleshooting With A Voltmeter</u>	Page
Developing The Fundamentals For Locating An "Open" In A Circuit...	6B-1
Physical Inspection	6B-2
Structure-Ground (metal airframe of the aircraft)	6B-2
Faulty Connection.....	6B-2
Corrosion—The Hidden Enemy	6B-3
Open Circuit Breaker	6B-3
Broken Wire.....	6B-3
General Procedure For Locating the "Open": Figures 6B-B1 Through B4.....	6B-4
Wire Sizes And Plastic Insulated Colors.....	6B-5
Normal Series Circuit With Voltage Drops	6B-6
Examples:	
Resistors In Series Circuit 6B-A.....	6B-6

Lamps And Resistor Series Circuit 6B-B	6B-7
Lamps Parallel And Resistor In Series Complex Circuit 6B-C.....	6B-8
Normal And Faulted Circuits For Comparison.....	6B-9
Lamps Series Circuit 6B-D1—Condition: Normal.....	6B-9
Lamps Series Circuit 6B-D2—Condition: Open Lamp.....	6B-9
Lamps Series Circuit 6B-D3—Condition: Severely Corroded Ground Connection	6B-9
Lamps Series Circuit 6B-D4—Condition: Open Ground Wire	6B-9
Nav/Com Radio Circuit 6B-E1—Condition: Defective Radio.....	6B-10
Nav/Com Radio Circuit 6B-E2—Condition: Open Ground Wire	6B-10
Resistors Series Circuit 6B-F1—Condition: Open In Resistor R1	6B-11
Resistors Series Circuit 6B-F2—Condition: Open In Ground Wire	6B-11
Lamps Parallel Circuit 6B-G1—Condition: Open Wire Between Connector 2 and Lamp 2	6B-12
Lamps Parallel Circuit 6B-G2—Condition: Open Switch In ON Position	6B-13
Digital Clock Circuit 6B-H1—Condition: Normal.....	6B-14
Digital Clock Circuit 6B-H2—Condition: Severe Corrosion At Ground Connection	6B-14
LED And Resistor Series Circuit 6B-I1—Condition: "Blown" Fuse.....	6B-15
LED And Resistor Series Circuit 6B-I2—Condition: Open LED	6B-15
Solenoid Circuit 6B-J1—Condition: Open Solenoid.....	6B-16
Solenoid Circuit 6B-J2—Condition: Open Circuit Breaker	6B-16
Summary	6B-17

PART 7

Troubleshooting Components Using Analog Multimeters In Ohmic Mode; Digital Multimeters In Both Ohmic And Diode Modes

Developing The Fundamentals... 7-1

Using The Analog Multimeter In Ohmic Mode; Digital Multimeter In Both Ohmic And Diode Modes
Troubleshoot Electrical Components Using Multimeters..... 7-2, 3

What To Look For When Measuring An Electrical Component..... 7-4, 5

Five Basic Steps In Troubleshooting An Electrical Component

7-6

Checking A SPST Switch For A Fault, Using A Digital Multimeter In Ohmic Mode..... 7-7

Checking A Fuse For Fault, Using A Digital Multimeter In Ohmic Mode..... 7-8

Checking A Fusible Link For A Fault, Using A Digital Multimeter In Ohmic Mode

7-9

Checking An Incandescent Lamp For A Fault, Using A Digital Multimeter In Ohmic Mode

7-10

Checking A <u>Diode</u> For A Fault, Using A <u>Digital</u> Multimeter In <u>Diode</u> Mode	7-11
Checking A <u>Circuit Breaker</u> For A Fault, Using A <u>Digital</u> Multimeter In <u>Ohmic</u> Mode.....	7-12
Checking A <u>Diode</u> For A Fault, Using A Common <u>Analog</u> Multimeter.....	7-13
Checking A <u>LED</u> For A Fault, Using A <u>Digital</u> Multimeter In <u>Diode</u> Mode.....	7-14
Checking A <u>LED</u> For A Fault, Using A Sensitive Analog Multimeter.....	7-15
Checking A <u>Transistor</u> (NPN) For A Fault, Using A <u>Digital</u> Multimeter In <u>Diode</u> Mode.....	7-16
Checking A <u>Transistor</u> (NPN) For A Fault, Using A <u>Common</u> Analog Multimeter.....	7-17
Measurement Examples Of Common Components In <u>Various Electrical Conditions</u> , Using Both <u>Analog</u> And <u>Digital</u> Multimeters	7-18

Components Measured With A Digital Multimeter (DMM):

Lamp 5 Ω	7-19
Switch (SPST).....	7-20, 21
Quick Disconnect.....	7-22
Battery Terminal To Battery Post	7-23
Capacitor (polarized)	7-24
Wire (stranded)	7-25
Resistor 900 Ω	7-26
Inductor (choke) 165 Ω	7-27
Clock—Analog (3.2M Ω).....	7-28
Diode (silicon)	7-29
Light Emitting Diode (non-blinking).....	7-30
Transistor NPN	7-31
Transistor PNP	7-32
Measuring Solid-State Components With A <u>Common</u> Analog Multimeter:.....	7-33
Diode (silicon)	7-34
Diode (silicon).....	7-35
Transistor NPN	7-36, 37, 38
Summary	7-39

PART 8

<u>Troubleshooting With A Ohmmeter And Other Instruments</u>	Page
Developing Fundamentals For Troubleshooting "Shorted Circuits"...	8-1
Fundamentals of Locating The "Short-To-Ground" In Circuits	8-2

Defining The Infamous "Short-To-Ground" Circuit—What Is It?	8-2
General Types Of Shorts.....	8-2
Methods Used To Locate A Wire Section or Component That Has A "Short-To-Ground"	8-2
What Determines The Method Used?	8-3
Ohmmeter Method	8-4
Ohmmeter Method Normal Series Circuit 8-A1	8-5
Low Resistance Short Or Short-To-Ground Or Ground Fault.....	8-5
High Resistance Short.....	8-5
Procedure For Locating A "Short-To-Ground" In A Series Circuit 8-A3	8-6
Ohmmeter Method: Parallel Circuits 8-B1, 8-B2	8-7
Procedure For Locating A "Short-To-Ground" In A Parallel Circuit 8-B3	8-8
Procedure For Using Either The Fuse Or Circuit Breaker Method Circuit 8-C1 Through 8-C6	8-9, 10
Short Finder Method Circuit 8D	8-11
Observation Method (using our senses).....	8-11
Voltmeter, Test Light Or Buzzer Method Circuit 8-E1 Through 8-E7	8-12, 13, 14,
Test Light Method Circuit 8-F1 Through 8-F11.....	8-15, 16, 17, 18
Buzzer Method Figure 8A	8-19
How To Troubleshoot A Suspected Circuit Of Having A Short	8-20
Know How The Circuit Operates Normally Circuit 8-G1.....	8-21
How To Check An Electrical System, Suspect In Having A <u>High</u> Resistance "Short-To-Ground In Circuit 8-G2	8-22
Procedure 1: Troubleshooting A "Short" Circuit. Install Loadmeters In Circuit 8-G3	8-23
Procedure 2: Turn ON Master Switch, Remove Fuse, Open Circuit Breakers In Circuit 8-G4.....	8-24
Procedure 3: Turn OFF all Light Switches In Circuit 8-G5.....	8-25
Procedure 4: Turn ON Over Head Lights Switch In Circuit 8-G6.....	8-26
Procedure 5: Turn ON Taxi Light Switch In Circuit 8-G7.....	8-27
Procedure 6: Turn ON Navigation Lights' Switch In Circuit 8-G8.....	8-28
Procedure 7: Disconnect All Necessary Wire Sections As In Circuit 8-G9.....	8-29
Procedure 8: Connect Breaker 2 Navigation Wire To Navigation Switch in Circuit 8-G10.	8-30
Procedure 9: Connect Nav. Lights' Wire To The Output Side Of Breaker. 2 In Circuit. 8-G11.....	8-31
Procedure 10: Connect Navigation lights' Switch To Terminal Strip In Circuit 8-G12.....	8-32
Procedure 11: Connect The White Navigation light Switch To Terminal Strip In Circuit 8-G13.....	8-33
The Short Has Been Found—Repair Discussion.....	8-34

PART 9

The Ammeter And The Loadmeter

.Page

Developing The Fundamentals...	9-1
The Ammeter	9-2
What Is An Ammeter	9-2
Basic Construction Of An Ammeter (analog)	9-2
How Does An Ammeter Work (basic operation)	9-2
Introduction To The Many Forms Of The Ammeter	9-3
How The Ammeter And Loadmeter Are Used In Troubleshooting	9-4
Types Of Multi-Meters: Analog, Digital, Hybrid, Clamp-On	9-5
General Types of Multimeter Displays.....	9-6
Multimeter And Single-Function Type Meters: Multimeters, Single-Functions, Ammeters	9-7
How Ammeters Are Typically Connected To DC Generator Charging Systems	9-8
Loadmeters: Purpose And How They Are Typically Connected To DC Charging Systems	9-9
How Loadmeters Are Typically Connected To DC <u>Generator</u> Charging Systems Circuit 9-A2.....	9-10
How Ammeters Are Typically Connected To DC <u>Alternator</u> Charging Systems Circuit 9-A3.....	9-10
How Loadmeters Are Typically Connected To DC Alternator Charging Systems Circuit 9-A4	9-11
Types Of Shunts Connected To Amp And Loadmeters: Externally Shunted Circuit. 9-B1, 9-B2	9-12
Internally Shunted Circuit. 9-B3, B4, B5	9-12
Types Of Meter Connections To A Circuit: Test Lead, Panel Mount, Clamp-On	9-13
Typical Digital Multimeter and Clamp-On.....	9-14
Panel-Mount Type Ammeters And Loadmeters	9-15
Ammeter And Loadmeter Adjustments	9-15
How Ammeters And Loadmeters Are Typically Connected To The Circuit	9-16
Ammeters Or Loadmeters As Part Of The Circuit 9-C1 Though 9-C7	9-16, 17, 18
Maintaining Proper Polarity Circuit 9-D1	9-19
"Electrically Facing" And "Physically Facing" Of A Meter With Respect To The Circuit's Polarity...	9-20
Ammeters Require Circuit Power And Their Connections In Series With the Circuit.....	9-21
Example Of Incorrect Hook Up Circuit 9-E1, 9-E2	9-22
Summary	9-23
How To Connect An Internally And Externally Shunted Voltage Or Amperage Loadmeter	9-24
How To Connect Clamp-On Meters To A Single Wire Circuit.....	9-25
How To Connect Clamp-On Meters To A Two Wire Circuit	9-26
Direction Of Magnetic Field Using Fleming's Right-Hand Rule For Conventional Current Flow.....	9-27

PART 10

The Generator, Alternator And Voltage Regulator

Page

Developing the Fundamentals...

10-1

Generators With 3-Unit Voltage Regulators: How They Are Connected, How They Work.....	10-2
Generators: How They Produce Electricity Circuit 10-C, D, E.....	10-3, 4
Using The Oscilloscope To See The Actual Electrical Voltage Output Of A Generator.....	10-5
Troubleshooting With An Oscilloscope: DC Generator (Type "A") With 3-Unit Regulator.....	10-6
Generator Not Producing Voltage: DC Generator (Type "B") With 3-Unit Regulator.....	10-7
Troubleshooting With An Oscilloscope: DC Generator (Type "B") With 3-Unit Regulator.....	10-8
Troubleshooting The Generator's "A" Or "B" Field Using An Analog Multimeter.....	10-9
Troubleshooting the Generator's Type "A" Field Using An Analog Multimeter.....	10-10
Troubleshooting the Generator's Type "B" Field Using A Digital Multimeter.....	10-11
Prior To Dismantling An "A" Type Generator, You Can Perform A Full-Field Excitation Test.....	10-12
Prior To Dismantling A "B" Type Generator, You Can Perform A Full-Field Excitation Test.....	10-13
How To Convert A Generator To A State-State Regulator Having a 3-unit Electromech. Relay.....	10-14
Troubleshooting the Generator's Type "A" Or "B" Armature Using A Growler.....	10-15
Troubleshooting Generator's Type "A" Or "B", Armature Short-To-Shaft Using A Digital Multimeter...	10-16
Generator Brushes Seating To Commutator.....	10-17
Brushes, Springs, Levers And Gage To Measure Spring Tension On Generator Brushes.....	10-18
A General Summary Of A 3-Unit Electromechanical Voltage Regulator Operation.....	10-19, 20
Generator Summary.....	10-21
Alternators And Generators Compared.....	10-22
Alternator's Rear Housing Electrical Connections.....	10-23
How To Static Test The Alternator's Rotor Circuits 10-I1, I2.....	10-24
How To Static Test The Alternator's Stator Circuits 10-J1, J2, J3,	10-25
How To Static Test The Alternator's Diode Block Circuit 10-H1, H2, H3.....	10-26
How To Static Test The Alternator's Diodes and Brushes Ckts. 10-H4, 5, Figs. 10J-1, 2, 3, 4, 5, 6...	10-27
Rough Capacitor Check Using An Analog Meter Circuits 10-J1, J2, J3, J4.....	10-28
Alternator's Solid-State Regulator—External View Figures 10-K1, 10-K2.....	10-29
Generic Solid-State Voltage Regulator Schematic Using A Generalized Operation.....	10-30
How To Check A Typical Solid-State Voltage Reg. (S.I. Series) Ckts. 10-L1, 2, 3, 4, 5.....	10-31, 32, 33
Troubleshooting Results Of A New S.I. Solid-State Regulator.....	10-33
How To "Flash" The Field (rotor) Of An Alternator (S.I. Series).....	10-34
How To Perform Full-Field Excitation To The Rotor (S.I. Series Alternator).....	10-35

Alternator (S.I. Series) Three Wire Charging Circuit 10-N1.....	10-36
Actual Rendition Of Alternator (S.I. Series) Three Wire Charging Circuit, 10-N1, Output As Shown By An Oscilloscope	10-37
Identify The Type Of Numbered Circuits.....	10-38
Identify The Type Of Numbered Circuits—Answers.....	10-39
Updating An Alternator To An External Solid-State Voltage Regulator.....	10-40
Using an Oscilloscope To Diagnose Alternator Fault—Open, No Capacitor, Shorted.....	10-41
A Shorted Alternator Capacitor While Charging—Consequences.....	10-42
Using an Oscilloscope To Diagnose Alternator Faults—Open Diode.....	10-43
Using an Oscilloscope To Diagnose Alternator Faults—Partially Shorted Diode Signal.....	10-44
Using an Oscilloscope To Diagnose Alternator Faults—Shorted Diode Or Shorted Stator.....	10-45
Using The "I A S F" Regulator to Check Alternator Voltage Output.....	10-46
How To Flash The Field (rotor) Of An Alternator.....	10-47
Summary.....	10-48

Introduction To Using A Combination Of Constant Voltage Section, Voltmeter and Ohm's Law To Determine A Voltage


In the following circuit voltage drops, as measured by each connected digital meter, are displayed in each meter's respective window. The voltage next to each lamp and resistor is its voltage drop created by the battery pushing current through each of the load's resistance. In the ANSWERS AND EXPLANATIONS column of each Circuit, you will find detailed and diverse reasons elucidating the concepts of the CONSTANT VOLTAGE SECTION (C.V.S.), its SEGMENTS and its IDENTICAL ELECTRICAL POINTS (I.E.P.s).

WHAT TO LOOK FOR WHILE STUDYING THE FOLLOWING FIVE CIRCUITS

1. Begin each Circuit by getting an overview of the circuit's operation.
2. Carefully locate, identify and qualify C.V.S.s, their SEGMENTS and their I.E.P.s.
3. Make note of how each load is connected to another and how they are connected to the power supply. In Circuits, loads are in series with each other or are in parallel with each other. Make note of that: is the load or loads in parallel or series with the power supply. Complex circuits are a combination of both series and parallel.
4. Watch for junctions and somewhat subtle connections. Remember, junctions divide current, but voltage remains the same at that point (with respect to ground).
5. Observe where the two test probes of the meter are placed in reference to each load. Are the probes along the load's C.V.S.? This will give you the same answer as if the probes were directly connected across that load. Look at the polarity of the probes with respect to the polarity of the load. Do the probes match or are they reversed with respect to the load's polarity? If the probes are reversed, the meter will display a negative voltage reading. This is not a problem; just reverse the leads.
6. Look at the positions of the controls such as switches, rheostats, potentiometers, etc. Remember, it is the position of the controls that will determine the voltage drops in the circuit. For Circuit, if a switch, rheostat, or potentiometer were turned OFF (open), it will change all your answers as compared to their being turned ON.
7. Compare your reasoning for the measured voltage with that stated in the ANSWERS AND EXPLANATION column that follows each of the five circuits. If your answer is not the same as that which is given, it may be because there are a number of different ways these concepts (C.V.S., SEGMENT, I.E.P.) can be explained or justified and still be correct. If your explanation does not match the one given, continue farther down the answer column and you may come across a similar situation, but with a reason that does match yours. More important, it is the essence of your answer that should be similar to mine, not your exact wording. If any of your answers are incorrect—you should redo them.
8. Once you are satisfied that you understand the CONSTANT VOLTAGE SECTION concept and all that it entails from each of the five Circuits, move on to PART 6.

Identifying Voltages Through The Combined Use Of C.V.S.s, Their Segments, Their I.E.P.s And A Voltmeter: Circuit 5-A1


Circuit 5-A1

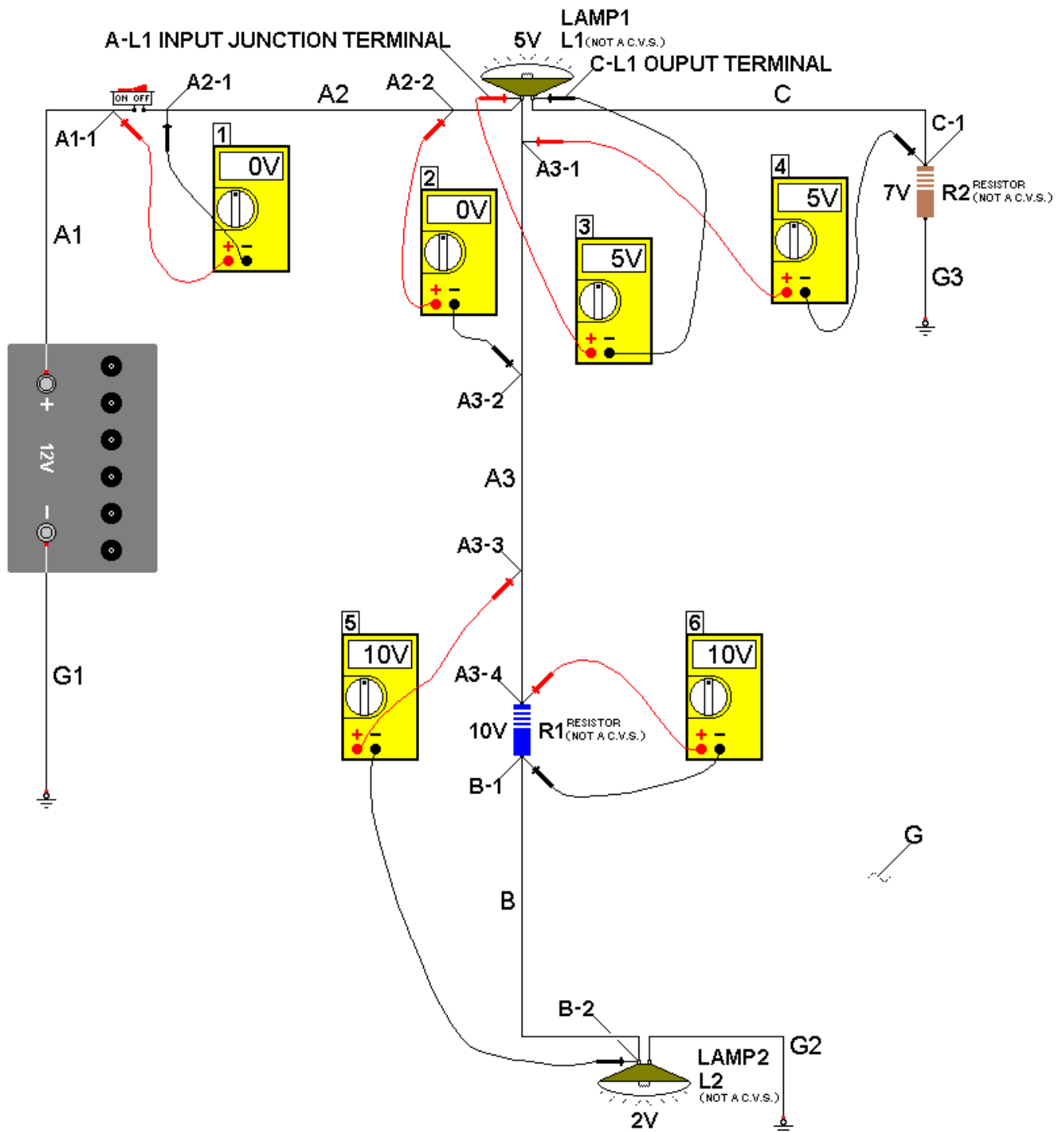

Meter No.	Voltage Reading	<u>Circuit 5-A1: Answers And Explanations</u>
1	0v	The resistance between the two probes of the meter is zero with the switch ON (closed). If either "I" or "R" were zero, the voltage is zero ($E = I \times R$). Although current is flowing between these two points, there is no significant resistance to create a voltage drop. Since both probes of the meter are located on the same C.V.S. "A" (A1-1 and A2-1), these probes are on Identical Electrical Points; therefore there is no voltage drop between them.
2	0v	The rocker switch and L1's input junction terminal interconnect three "A" sections of wire A1, A2, and A3. They are extensions of the positive terminal of the battery—they act as one with 12v all along their interconnected length with respect to ground. Since the section of wire between the two probes of Meter 2 is part of C.V.S. "A" and it has no significant resistance, the voltage will be zero.
3	5v	There will be a voltage drop, since there is resistance between the two probes (points) of the meter, in this case 5v. Because of this resistance, the two points are not identical. Since current is flowing through the resistance of lamp L1, a voltage drop is created. If current and resistance are both something other than zero, a voltage drop is formed ($E = I \times R$). In addition, the probes of the meter are on two different C.V.S.s, ("A" and "C"), which is caused by the lamp's resistance. Consequently, the meter will read the potential difference between these two points.
4	5v	The positive probes of Meters 3 and 4 are located on common Identical Electrical Points (I.E.P.s) of C.V.S. "A"—there is no resistance between these two points, they are the same. Using the same reasoning, the two negative probes of Meters 3 and 4 are also located on common electrical points of C.V.S. "C"—there is no resistance between them also. Since the probes (positive and negative) of Meter 4 are located on the same two I.E.P.s as Meter 3's probes (positive and negative), both meters will read the same 5v across lamp L1's resistance.
5	10v	The positive probes of Meters 5 and 6 are located on common Identical Electrical Points of C.V.S. "A"—there is no resistance between those two points, they are the same. Using the same reasoning, the two negative probes of Meters 5 and 6 are also located on common electrical points of C.V.S. "B"—there is no resistance between them also. Consequently, since the probes of Meter 6 are located on the same two points as the probes of Meter 5, both meters will read the same voltage.
6	10v	Since there is resistance between the two probes of Meter 6, there will be a voltage drop, in this case 10v. Because of this resistance created by the resistor R1, the two points where the probes are located are not identical. Since current is flowing through this resistance, a voltage drop is created. If current and resistance are both something other than zero, a voltage drop is formed ($E = I \times R$). In addition, the meter probes are on two different C.V.S.s; the meter will read the potential difference between C.V.S. "A" and C.V.S. "B".

Identifying Voltages Through The Combined Use Of C.V.S.s, Their Segments, The I.E.P.s And A Voltmeter: Circuit 5-A2

Circuit 5-A2

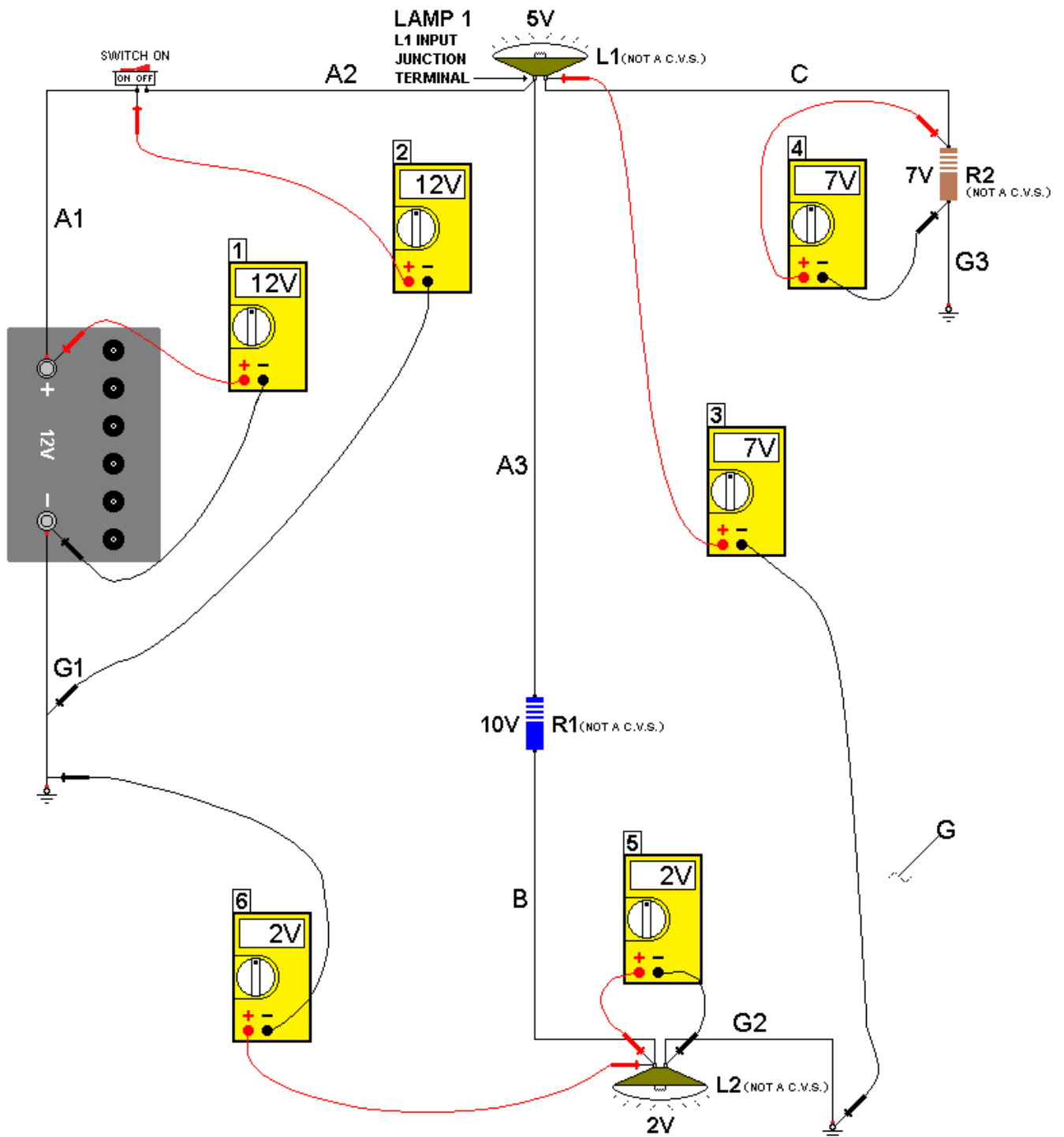

Meter No.	Voltage Reading	<u>Circuit 5-A2: Answers And Explanations</u>
1	12v	The meter's positive and negative probes are directly connected to each of the battery's positive and negative terminals, respectively; therefore the meter measures 12v.
2	12v	The switch's input terminal, where the meter's positive probe is connected, is an extension of the battery's positive terminal, and it is an Identical Electrical Point (I.E.P.) of C.V.S. A1. The ground connection is an extension of the battery's negative terminal, and it is an I.E.P. of C.V.S. G2.
3	7v	Meters 3 and 4 are both measuring the same resistor R2. Even though the probes of Meter 3 are physically located elsewhere on the circuit, electrically Meter 3's probes are located on the same two C.V.S.s as Meter 4's. The positive probes of Meters 3 and 4 are located on identical electrical points of C.V.S. "C"—there is no resistance between these two points, therefore they are the same. Using the same reasoning, the two negative probes of Meters 3 and 4 are also located on common C.V.S.s G3 and G4—there is no resistance between them also. Consequently, since the probes (positive and negative) of Meter 3 are located on the same two C.V.S.s as the probes (positive and negative) of Meter 4's, Meter 4 will read the same voltage.
4	7v	Since there is resistance (R2) between the two probes of the meter, there will be a voltage drop, in this case 7v. Because of this resistance, the two points where the probes are located are not identical. Since current is flowing through this resistance, a voltage drop is created. If current and resistance are both something other than zero, a voltage drop is present. $E = I \times R$
5	2v	There will be a voltage drop, since there is resistance between the two probes of the meter, in this case 2v. Because of this resistance created by the filament, which is located between the probes of the meter, the two points are not identical. Since current is flowing through a resistance, a voltage drop exists. If current and resistance are both something other than zero, a voltage drop is created. $E = I \times R$
6	3v	Meters 5 and 6 are both measuring the same lamp, L2. Meter 6's positive probe is located on the same physical and electrical point as meter 5's. Even though Meter 6's negative probe is physically located at the battery's ground, electrically the battery's ground and the lamp's ground are electrically the same point. Note: The three grounds in this circuit are connected electrically through the metal structure of the aircraft, G1. The negative terminal of the battery is connected to a heavy cable, which in turn is connected to the metal structure of the aircraft, which now becomes the common return for all currents back to the system's power supply.

Identifying Voltages Through The Combined Use Of C.V.S.s, Their Segments, Their I.E.P.s And A Voltmeter: Circuit 5-B

Circuit 5-B

